

IT 1204
Section 3.0

Boolean Algebra and Digital Logic



Boolean Algebra



Logic Equations to Truth Tables

$$X = A.\overline{B} + \overline{A}.B + AB$$

A	B	X
0	0	
0	1	
1	0	
1	1	

Sum of Products

- The **OR** operation performed on the products of the **AND** operation
- Fill the corresponding cells with **1** for each product, the other cells with **0**

$$X = (A.B) + (\bar{A}.\bar{B}) + (\bar{A}.B)$$

$$A = 1, \bar{A} = 0$$

$$B = 1, \bar{B} = 0$$

A	B	X
0	0	1
0	1	1
1	0	0
1	1	1

Product of Sums

- The **AND** operation performed on the sums of the **OR** operation
- Fill the corresponding cells with **0** for each sum, the other cells with **1**

$$Y = (\bar{A} + \bar{B}).(\bar{A} + B)$$

$$A = 0, \bar{A} = 1$$

$$B = 0, \bar{B} = 1$$

A	B	X
0	0	1
0	1	1
1	0	0
1	1	0

Truth Tables to Logic Equations

A	B	X
0	0	1
0	1	1
1	0	0
1	1	0

- Sum of Products - consider 1s
 - Consider A=1,B=1

$$X = (\bar{A}\bar{B}) + (\bar{A}B)$$

- Product of sums – consider 0s
 - Consider A=0,B=0

$$X = (\bar{A} + B).(\bar{A} + \bar{B})$$

Your Turn: Exercise1

- Convert the following equation which is in the form of Product-of-sums into the form of Sum-of-products

$$f(ABCD) = (A + \bar{B} + C)(\bar{A} + B + \bar{C} + \bar{D})(\bar{A} + \bar{B} + D)(A + \bar{C})$$

Answer: Exercise1

$$f(ABCD) = (A + \bar{B} + C)(\bar{A} + B + \bar{C} + \bar{D})(\bar{A} + \bar{B} + D)(A + \bar{C})$$

$$f(ABCD) = (A + \bar{B} + C)(\bar{A} + B + \bar{C} + \bar{D})(\bar{A} + \bar{B} + D)(A + \bar{C})$$

$$f(ABCD) = (A + \bar{B} + C) + (\bar{A} + B + \bar{C} + \bar{D}) + (\bar{A} + \bar{B} + D) + (A + \bar{C})$$

$$f(ABCD) = (\bar{A}.\bar{B}.\bar{C}) + (\bar{A}.\bar{B}.\bar{C}.D) + (\bar{A}.\bar{B}.D) + (\bar{A}.\bar{C})$$

$$f(ABCD) = (\bar{A}.B.\bar{C}) + (A.\bar{B}.C.D) + (A.B.\bar{D}) + (\bar{A}.C)$$

Boolean Postulates

$$0 \cdot 0 = 0$$

$$1 + 1 = 1$$

$$0 + 0 = 0$$

$$1 \cdot 1 = 1$$

$$1 \cdot 0 = 0 \cdot 1 = 0$$

$$1 + 0 = 0 + 1 = 1$$

Laws of Boolean Algebra

- **Commutative Law**

- $A + B = B + A$

- $A B = B A$

- **Associate Law**

- $(A + B) + C = A + (B + C)$

- $(A B) C = A (B C)$

Laws of Boolean Algebra

- **Distributive Law**
 - $A (B + C) = A B + A C$
 - $A + (BC) = (A + B) (A + C)$

- **Identity Law**
 - $A + A = A$
 - $A . A = A$

Laws of Boolean Algebra

- **Redundancy Law**

- $A + AB = A$

- $A(A + B) = A$

- **Demorgan's Theorem**

- $\overline{(A + B)} = \bar{A} \cdot \bar{B}$

- $\overline{(A \cdot B)} = \bar{A} + \bar{B}$

Laws of Boolean Algebra

- $A.B + A.\bar{B} = A$
 $(A + B)(A + \bar{B}) = A$
- $A + 0 = A$
 $A.0 = 0$

Laws of Boolean Algebra

- $1 + A = 1$
 $1 \cdot A = A$
- $A + \overline{A} = 1$
 $A \cdot \overline{A} = 0$

Laws of Boolean Algebra

- $A + \bar{A}.B = A + B$
- $A(\bar{A} + B) = AB$

Implementation of Boolean Functions

- A Boolean function can be realised in either **SOP** or **POS** form
- At this point, it would seem that the choice would depend on whether the truth table contains more **1s** and **0s** for the output function
- The **SOP** has one term for each **1**, and the **POS** has one term for each **0**

Implementation of Boolean Functions

- However, there are other considerations:
 - It is generally possible to derive a simpler Boolean expression from truth table than either **SOP** or **POS**
 - It may be preferable to implement the function with a single gate type (NAND or NOR)

Implementation of Boolean Functions

- The significance of this is that, with a simpler Boolean expression, fewer gates will be needed to implement the function
- Methods that can be used to achieve simplification are:
 - Algebraic Simplification
 - Karnaugh Maps

Your Turn: Algebraic Simplification

- Simplify the following equation using Boolean algebra laws

$$f(ABC) = (A + \bar{B} + \bar{C})(A + \bar{B}C)$$

Answer: Algebraic Simplification

$$f(ABC) = (A + \overline{B} + \overline{C})(A + \overline{BC})$$

$$f(ABC) = AA + A\overline{BC} + A\overline{B} + \overline{B}\overline{BC} + A\overline{C} + \overline{BC}\overline{C}$$

$$f(ABC) = A(1 + \overline{BC} + \overline{B} + \overline{C}) + \overline{BC} + \overline{BC}\overline{C}$$

$$f(ABC) = A + \overline{BC}$$

Karnaugh Maps

- For purposes of simplification, the Karnaugh map is a convenient way of representing a Boolean function of a small number (up to 4 to 6) of variables
- The map is an array of 2^n squares, representing the possible combinations of values of n binary variables

Karnaugh Maps

- The map can be used to represent any Boolean function in the following way:
 - Each square corresponds to a unique product in the **sum-of-products** form.
 - With a **1** value corresponding to the variable and a **0** value corresponding to the **NOT** of that variable


Karnaugh Maps: 2 Values

B \ A	0	1
0	0	1
1	1	1

$$X = A.\bar{B} + \bar{A}.B + AB$$

Karnaugh Maps: 2 Values

 - The $A\bar{B}$ corresponds to the fourth square in the Figure
- For each such production in the function, 1 is placed in the corresponding square



$$F = A\bar{B} + \bar{A}B$$

Karnaugh Maps: 3 Values

C \ AB	00	01	11	10
0	1	1	0	0
1	0	0	1	1

$$X = A.\bar{B}.C + \bar{A}.B.\bar{C} + A.B.C + \bar{A}.\bar{B}.\bar{C}$$

Karnaugh Maps: 4 Values

CD \ AB	00	01	11	10
00	1	0	1	1
01	0	1	1	0
11	0	1	1	0
10	0	1	0	1

$$X = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D + \overline{A}B\overline{C}D$$

Karnaugh Maps: Exercise 1

- Simplify the following Karnaugh Map using Boolean equations (Write your answers in both **SOP** and **POS**)

C \ AB	00	01	11	10
0	0	1	0	0
1	1	1	0	1

Karnaugh Maps: Answer

$$(\overline{A}.\overline{B}.\overline{C}) + (\overline{A}.\overline{B}.C) + (\overline{A}.B.C) + (A.\overline{B}.C) \iff \overline{A}B + \overline{B}C$$

$$(A + B + C).(\overline{A} + \overline{B} + C).(\overline{A} + B + \overline{C}).(\overline{A} + \overline{B} + \overline{C}) \iff (B + C).(\overline{A} + \overline{B})$$

C \ AB	00	01	11	10
0	0	1	0	0
1	1	1	0	1


Karnaugh Maps: Exercise 2

- Simplify the following Karnaugh Map using Boolean equations (Write your answers in both **SOP** and **POS**)

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	0	1	0
10	1	0	0	1

Karnaugh Maps: Answer
 
$$\overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D}$$



$$\overline{B}\overline{D} + \overline{B}C\overline{D} + A\overline{B}\overline{D}$$

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	0	1	0
10	1	0	0	1

The Karnaugh map shows the following groupings:


- Red boxes highlight the minterms $\overline{A}\overline{B}\overline{C}\overline{D}$, $\overline{A}\overline{B}C\overline{D}$, $\overline{A}B\overline{C}\overline{D}$, and $\overline{A}BC\overline{D}$, which simplify to $\overline{B}\overline{D}$.
- Blue boxes highlight the minterms $\overline{A}\overline{B}\overline{C}\overline{D}$, $\overline{A}\overline{B}C\overline{D}$, $\overline{A}B\overline{C}\overline{D}$, and $\overline{A}BC\overline{D}$, which simplify to $\overline{B}\overline{D}$.
- Red boxes highlight the minterms $\overline{A}\overline{B}\overline{C}\overline{D}$, $\overline{A}\overline{B}C\overline{D}$, $\overline{A}B\overline{C}\overline{D}$, and $\overline{A}BC\overline{D}$, which simplify to $\overline{B}\overline{D}$.
- Blue boxes highlight the minterms $\overline{A}\overline{B}\overline{C}\overline{D}$, $\overline{A}\overline{B}C\overline{D}$, $\overline{A}B\overline{C}\overline{D}$, and $\overline{A}BC\overline{D}$, which simplify to $\overline{B}\overline{D}$.

Karnaugh Maps: Answer

$$(A + \bar{B} + C + D).(\bar{A} + \bar{B} + C + D).(A + \bar{B} + \bar{C} + D).(\bar{A} + \bar{B} + \bar{C} + D).$$

$$(A + B + C + \bar{D}).(A + B + \bar{C} + \bar{D}).(\bar{A} + B + C + \bar{D}).(\bar{A} + B + \bar{C} + \bar{D}).$$

$$(A + \bar{B} + \bar{C} + \bar{D})$$

 


$$(\bar{B} + D).(B + \bar{D}).(A + \bar{C} + \bar{D})$$

CD \ AB	00	01	11	10
00	1	0	0	1
01	0	1	1	0
11	0	0	1	0
10	1	0	0	1

Simplified Labeling of Karnaugh Maps

- The labeling used in figure emphasizes the relationship between variables and the rows and columns of the map

 - The two rows embraced by the symbol **A** are those in which the variable **A** has the value **1**; the rows not embraced by the symbol **A** are those in which **A** is **0**




Simplified Labeling of Karnaugh Maps

- Once the map of a function is created, we can often write a simple algebraic expression for it by noting the arrangement of the **1s** on the map
- The principle is as follows:
 - Any two squares that are adjacent differ in only one of the variables
 - If two adjacent squares both have an entry of **1**, then the corresponding product terms differ in **only one variable**
 - In such a case, the two terms can be merged by **eliminating that variable**

Simplified Labeling of Karnaugh Maps

- For example, in following FIGURE, the two adjacent squares correspond to the two terms $\bar{A}\bar{B}\bar{C}D$ and $\bar{A}\bar{B}CD$


 
- The function expressed is $\bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD = \bar{A}\bar{B}D$




Simplified Labeling of Karnaugh Maps

- This process can be extended in several ways:
 - First, the concept of adjacent can be extended to include wrapping around the edge of the map
 - Thus, the **top square of a column** is adjacent to the **bottom square**, and the **leftmost square of a row** is adjacent to the **rightmost square**
 - Second, we can group not just 2 squares but 2^n adjacent squares, that is, 4, 8, etc



Your turn: Karnaugh Maps

  


Answer: Karnaugh Maps

 

Your turn: Karnaugh Maps

 
 


Answer: Karnaugh Maps

 


$\bar{A}B\bar{D}$

Your turn: Karnaugh Maps

 
 


Answer: Karnaugh Maps

 


$\bar{A}\bar{B}$



Your turn: Karnaugh Maps

  


Answer: Karnaugh Maps

 



Your turn: Karnaugh Maps

  


Answer: Karnaugh Maps

 

Your turn: Karnaugh Maps

  


Answer: Karnaugh Maps

 


Simplified Labeling of Karnaugh Maps

- In attempting to simplify, first look for the largest grouping possible:
 - When you are circling groups, you are allowed to use the same **1** more than **once**
 - If any isolated **1s** remain after the groupings, then each of these is circled as a group of **1s**
 - Finally, before going from the map to a simplified Boolean expression, any group of **1s** that is **completely overlapped by other groups can be eliminated**

Karnaugh Maps: Overlapping Groups

 

$$F = \bar{A}B + B\bar{C}$$

 


$$F = B\bar{C}D + ACD$$

Your turn: Karnaugh Maps

CD

	0	0	0	0
	0	0	0	1
AB	1	1	0	1
	1	1	1	1

 

Answer: Karnaugh Maps

		CD			
		00		01	
AB	0	0	0	0	
	0	0	0	1	
	1	1	0	1	
	1	1	1	1	

$$F = A\bar{C} + A\bar{B} + BCD$$


$$F = (A+C).(A+B).(\bar{B}+\bar{C}+\bar{D})$$

Drawing a Circuit


Sum-of-Products Expression

$$\bar{A} \bar{B} \bar{C} + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B \bar{C} + A B C$$

Digital Logic Circuit

 


Drawing a Circuit

 

Drawing a Circuit

$$B+AC$$

 

Logic Operators




Logic Operations

- Basic logic operators and logic gates
- Boolean algebra
- Combinational Circuits
- Basic circuit design

Basic Logic Operators and Logic Gates

- AND
- OR
- NOT
- XOR (Exclusive OR)
- NOR
- NAND
- XNOR

Buffer

 

A	B
0	0
1	1

AND Operation


- . Operator
- ^ Operator
- $A . B = A \wedge B$



A	B	A . B
0	0	0
0	1	0
1	0	0
1	1	1

OR Operation

 - $+$ Operator
- \vee Operator
- $A + B = A \vee B$




A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

NOT Operation

- \sim Operator
- \neg Operator

$$\bar{A} = \neg A = \sim A = A'$$

A	A'
0	1
1	0

 

XOR Operation

- \oplus Operator

$$A \oplus B$$



A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

NAND Operation

$$\overline{(A.B)} = (A.B)'$$



A	B	$\overline{(A.B)}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR Operation

$$\overline{(A + B)} = (A + B)'$$



A	B	$\overline{(A + B)}$
0	0	1
0	1	0
1	0	0
1	1	0

XNOR Operation

$$\overline{(A \oplus B)}$$



A	B	$\overline{(A \oplus B)}$
0	0	1
0	1	0
1	0	0
1	1	1


Drawing Logic Gates

- In addition to the basic gates, gates with 3,4, or more inputs can be used

E.g. $x + y + z$ can be implemented with a single **OR** gate with 3 inputs


Drawing Logic Gates

$$X = (A + B)C$$

 


Drawing Logic Gates

$$X = A + (B.C) + \bar{D}$$

 


Drawing Logic Gates

$$X = (A.B) + (\overline{A}.C)$$

 


Drawing Logic Gates
 
$$X = \overline{(A + B)} \cdot (C + D) \cdot \overline{C}$$




Reducing Logic Gates

 - Reducing the number of inputs
 - The number of inputs to a gate can be reduced by connecting two (or more) inputs together
 - The diagram shows a 3-input **AND** gate operating as a 2-input **AND** gate



Reducing Logic Gates

 - Reducing the number of inputs
 - Reducing a NOT gate from a NAND or NOR gate
 - The diagram shows this for a 2-input **NAND** gate



Logic Gates

- Typically, not all gate types are used in implementation
 - Design and fabrication are simpler if only one or two types of gates are used
 - Therefore, it is important to identify *functionally complete* sets of gates
 - This means that any **Boolean function** can be implemented using only the gates in the set

Logic Gates

- The following are functionally complete sets:
 - **AND, OR, NOT**
 - **AND, NOT**
 - **OR, NOT**
 - **NAND**
 - **NOR**

Logic Gates

- **AND, OR, and NOT** gates constitute a functionally complete set, since they represent the 3 operations of *Boolean algebra*
- For the **AND** and **NOT** gates to form a functionally complete set, there must be a way to synthesize the **OR** operation from the **AND** and **NOT** operations

$$A + B = \overline{\overline{A} \cdot \overline{B}}$$

$$A \text{ OR } B = \text{NOT} ((\text{NOT } A) \text{ AND } (\text{NOT } B))$$

Logic Gates

- Similarly, the **OR** and **NOT** operations are functionally complete because they can be synthesize the **AND** operation

$$A \cdot B = \overline{\overline{A} + \overline{B}}$$


$$A \text{ AND } B = \text{NOT}((\text{NOT } A) \text{ OR } (\text{NOT } B))$$

Logic Gates

- The **AND**, **OR** and **NOT** functions can be implemented solely with **NAND** gates, and the same thing for **NOR** gates.
- For this reason, digital circuits can be, and frequently are, implemented solely with **NAND** gates or solely with **NOR** gates


Logic Gates

 - The diagram shows how the **NOT** function can be implemented solely with **NAND** gate




Logic Gates

 - The diagram shows how the **AND** function can be implemented solely with **NAND** gate




Logic Gates

 - The diagram shows how the **OR** function can be implemented solely with **NAND** gate




Logic Gates

 


Your turn

 - Draw a diagram that shows how the **NOT** function can be implemented solely with **NOR** gate




Logic Gates

 - The diagram shows how the **NOT** function can be implemented solely with **NOR** gate




Your turn

 - Draw a diagram that shows how the **OR** function can be implemented solely with **NOR** gate




Logic Gates

 - The diagram shows how the **OR** function can be implemented solely with **NOR** gate




Your turn

 - Draw a diagram that shows how the **AND** function can be implemented solely with **NOR** gate




Logic Gates

 
- The diagram shows how the **AND** function can be implemented solely with **NOR** gate




Substituting Gates in an Logic System

 

Substituting Gates in an Logic System

 

Substituting Gates in an Logic System

 

Combinational Circuits




Combinational Logic

- Also called combinatorial logic
- A type of logic circuit whose output is a function of the present input only

Half Adder

 - Finds the sum of two bits
- The sum can be found using the XOR operation and the carry using the AND operation




Full Adder

- We can change our half adder into to a full adder by including gates for processing the carry bit
- The truth table for a full adder is:

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Converting a Half Adder into a Full Adder

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Ripple-carry Adder (I)

 - Just as we combined half adders to make a full adder, full adders can be connected in series
 - The carry bit “ripples” from one adder to the next; hence, this configuration is called a ripple-carry adder




Ripple-carry Adder (II)

 

Adder

 
Adders (and other arithmetic circuits) are usually drawn like this in block diagrams




collections of parallel, related wires like this are known as buses; they carry multi-bit values between components

Decoder

 - Selects a memory location according a binary value placed on the address lines of a memory bus
- Decoders with n inputs can select any of 2^n locations




2-to-4 Decoder

 


Multiplexer

 - A multiplexer does the opposite of a decoder
- Selects a single output from several inputs
 - The particular input chosen for output is determined by the value of the multiplexer's control lines
 - To select among n inputs, $\log_2 n$ control lines are needed




4-to-1 Multiplexer

 


Arithmetic

- Computers need to do more than just addition
 - arithmetic: + – * / %
 - logic: & | ~ << >>
- Need a circuit that can select operation to perform

Arithmetic Logic Unit (ALU)

 

Arithmetic Logic Unit (ALU)

 


Sequential Logic – Memory

Sequential Logic Circuits

- Combinational logic circuits are perfect for situations which require the immediate application of a Boolean function to a set of inputs
- But, here are times when we need a circuit to change its value with consideration to its current state as well as its inputs
 - These circuits have to “remember” their current state
- *Sequential logic circuits* provide this functionality

Sequencing Events

 
- Sequential logic circuits require a means by which events can be sequenced
 - State changes are controlled by clocks
 - A “clock” is a special circuit that sends electrical pulses through a circuit
 - Clocks produce electrical waveforms such as this one



- State changes occur in sequential circuits only when the clock ticks



Feedback in Sequential Logic Circuits

 - Sequential circuits rely on feedback to retain their state values
- Feedback in digital circuits occurs when an output is looped back to the input
 - Example,



If Q is 0 it will always be 0, if it is 1, it will always be 1

SR Flip-flop (Set-Reset) (I)

  


- The behavior of an SR flip-flop is described by a *characteristic table*
 - $Q(t)$ output at time t
 - $Q(t+1)$ output after the next clock pulse

S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined

SR Flip-flop: Block Diagram

 Flip-flops are often drawn like this in block diagrams



CK is read/write (“clock” because this input is connected to the computer’s processor clock)



SR Flip-flop (II)

- The SR flip-flop has three inputs: S, R and Q(t)
 - When both S and R are 1, the SR flip-flop is unstable

Present State			Next State
S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	undefined
1	1	1	undefined

JK Flip-flop (Jack Kilby)

  - Modified version of the SR flip-flop to provide a stable state when both inputs are 1




J	K	Q(t+1)
0	0	Q(t) (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

JK Flip-flop: Binary Counter

- The low-order bit is complemented at each clock pulse
- Whenever it changes from 1 to 0, the next bit is complemented, and so on through the other flip-flops


J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

 


D Flip-flop (Data)

- Fundamental circuit of computer memory
- Used to store 1 bit
- Can be implemented with gates
- Not combinatorial logic
 - because current output may depend on previous state
- Example of sequential logic
 - current output depends on inputs and prior output


D Flip-flop

 


D Flip-flop: Writing

 


D Flip-flop: Reading

 

D Flip-flop: Block Diagram

 

D Flip-flop: 4-bit Register

 


A register stores data inside the CPU




Memory

- Memory can store many bits independently
 - register banks contain many flip-flops
- Need to identify which bit (flip-flop) to read or write
- Give each flip-flop a unique number (address)


Memory: Circuit Diagram

 


Memory: Writing

 

Memory: Reading

 

Memory: 4-words, 3 bits/word

 

Summary (I)

- Computers are implementations of Boolean logic
- Boolean functions are completely described by Truth Tables
- Logic gates are small circuits that implement Boolean operators
- The basic gates are AND, OR and NOT
- The “universal gates” are NOR and NAND

Summary (II)

Computer circuits consist of combinational logic circuits and sequential logic circuits

- Combinational circuits produce outputs (almost) immediately when their inputs change
- Sequential circuits have internal states as well as combinations of input and output logic
 - The outputs may also depend on the states left behind by previous inputs
 - Sequential circuits require clocks to control their changes of state
 - The basic sequential circuit unit is the flip-flop

Thank You

